Documentation

About

- A simple light up LED greeting card

Components used

- Coin cell 3V battery
- Copper sheet
- LED (yellow)

Circuit diagram

